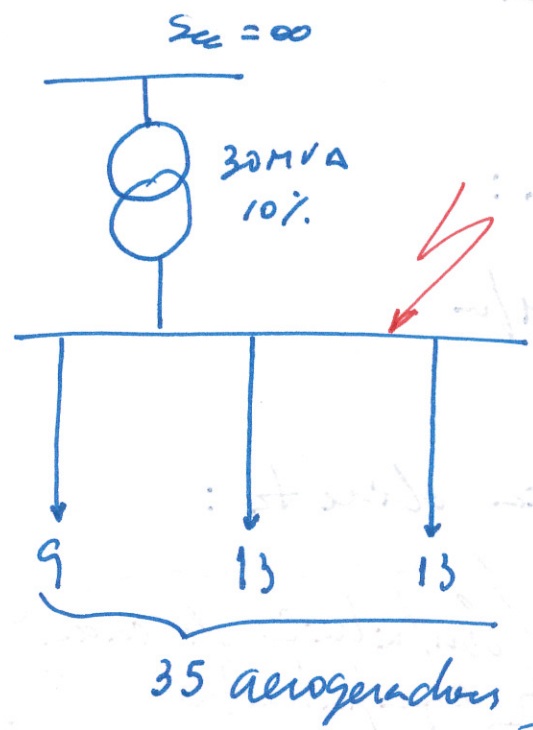


# CÁLCULO DA CORRENTE DE CURTO-CIRCUITO NA MT DE UM PARQUE EÓLICO:



Aerogerador:  
 $S = 0,895 \text{ MVA}$   
 $X_d'' = 29\%$

Transformador:  
 $S = 1 \text{ MVA}$   
 $u_{cc} = 6\%$

$S_T = 1 \text{ MVA}$

1 - Cálculo das impedâncias dos elementos da rede:

1.1. Transformador 30MVA:

$$X(lm) = \frac{10}{100} \cdot \frac{1}{30} = 3,33 \times 10^{-3} \text{ pu}$$

1.2. Aerogerador

$$X_d''(h) = \frac{29}{100} \times \frac{1}{0,895} = 0,324 \text{ pu}$$


1.3. Transformada

$$X = \frac{6}{100} \times \frac{1}{1} = 0,06 \mu$$

1.4. Acoplada + Transformada:

$$X = 0,324 + 0,06 = 0,384 \mu$$

2. Cálculo da impedância direta:

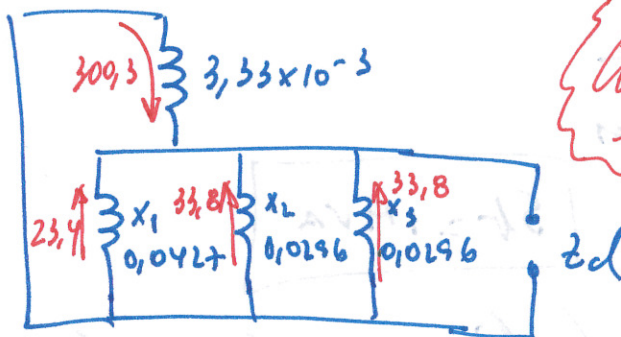


Contribuição de cada equipamento

$$X_1 = \frac{0,384}{9} = 0,0427$$

$$X_2 // X_3 = \frac{0,0296}{2} = 0,0148$$

$$X_2 = \frac{0,384}{13} = X_3 = 0,0296$$

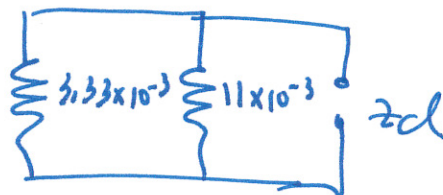
$$\frac{0,0427 \cdot 0,0148}{0,0427 + 0,0148} = 0,011$$




$$Z_d = 2,55 \times 10^{-3} \mu$$

# CÁLCULO SIMPLIFICADO

4

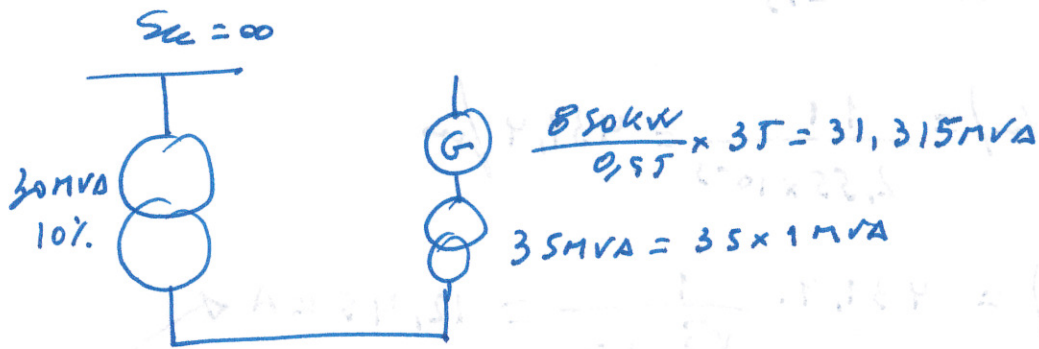


Conjunto aerogenerador + transformador:

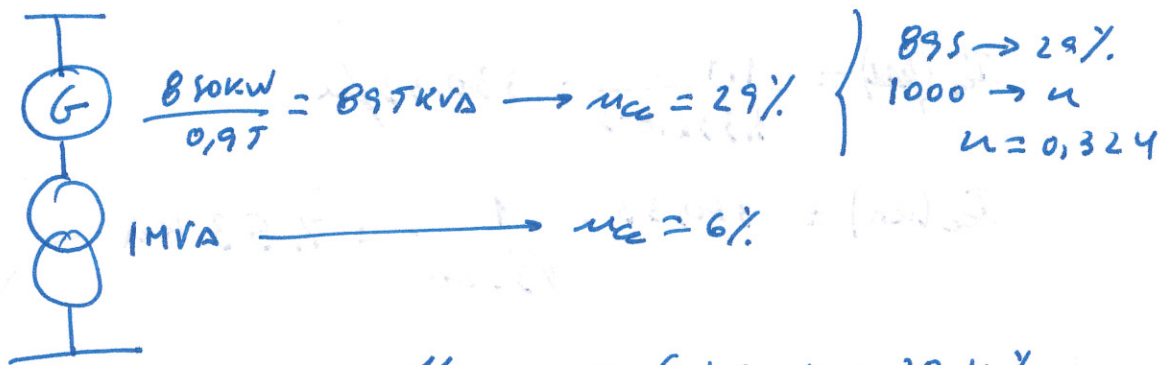

$$u_{c\text{TOTAL}} = 6 + 32,4 = 38,4\%$$

Paraando p/  $u_c = 10\%$ :
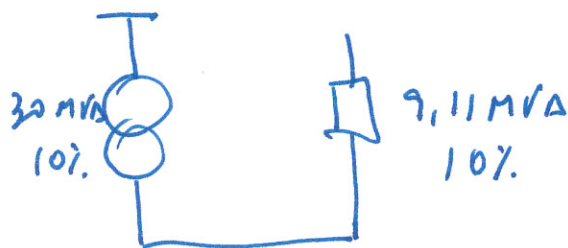
$$S'_{sc} = \frac{z'}{z} \times S_{sc} = \frac{10}{38,4} \times 35 = 9,11 \text{ MVA}$$



$$I_{sc} = \frac{39,11 \times 10^6 \times 100 \times 1,1}{\sqrt{3} \cdot 20 \times 10^3 \cdot 10} = 12,42 \text{ kA}$$

3 - Cálculo do  $I_{cTS}$ :

$$I_{cTS} (\mu) = \frac{1,1}{2,55 \times 10^{-3}} = 431,4 \mu$$

$$I_{cTS} (kA) = 431,4 \cdot \frac{1}{\sqrt{3} \cdot 20} = 12,45 kA$$

Contribuição da rede:

$$I_c (\mu) = \frac{1,1}{3,33 \times 10^{-3}} = 330,33 \mu$$

$$I_c (kA) = 330,33 \cdot \frac{1}{\sqrt{3} \cdot 20} = 9,53 kA$$

Contribuição dos aerogeradores + Turbina:


$$I_{cc} (\mu) = \frac{1,1}{11 \times 10^{-3}} = 100 \mu$$

$$I_{cc} (kA) = 100 \cdot \frac{1}{\sqrt{3} \cdot 20} = 2,89 kA$$

$\approx$   
 $+ = 12,42 kA$

# PANEL EÓLICO MEL 2
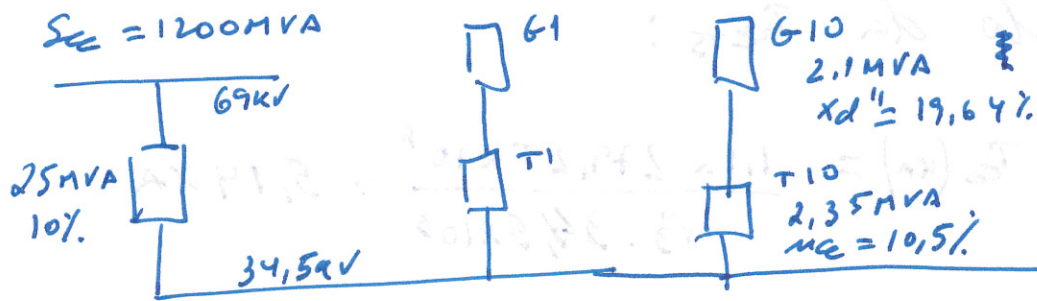
## CÁLCULO DAS CORRENTES DE CURTO-CIRCUITO ①



$$u_{cc}\% = \frac{25 \times 100}{1200} = 2,08\%$$

$$u_{cc\text{ TOTAL}} = 10 + 2,08 = 12,08\%$$

a) Contribuição da rede + transf. potência:  $\frac{25}{0,1208} = 206,95 \text{ MVA}$

b) Contribuição de 1 aerogerador + 1 transformador:

$$S_{cc} = \frac{1}{\frac{1}{10,69} + \frac{1}{22,38}} = 7,23 \text{ MVA}$$

$\frac{2,1 \times 100\%}{19,64\%}$        $\frac{2,35 \times 100\%}{10,5\%}$

c) Contribuição da rede + 10 aerogeradores:

$$206,95 + 10 \times 7,23 = 279,25 \text{ MVA}$$



d) Cálculo de  $I_{eTS}$ :

$$I_e (kA) = \frac{1,1 \times 279,25 \times 10^6}{\sqrt{3} \cdot 34,5 \times 10^3} = 5,14 kA$$